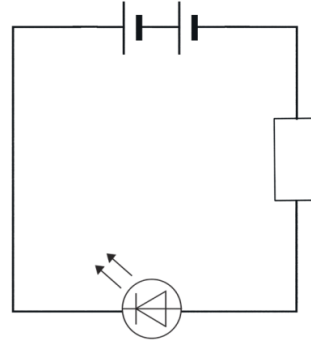


|     |          |          |          |          |          |   |
|-----|----------|----------|----------|----------|----------|---|
| Q1  | A        | B        | C        | D        | <b>E</b> | F |
| Q2  | A        | <b>B</b> | C        | D        | E        | F |
| Q3  | <b>A</b> | B        | C        | D        | E        | F |
| Q4  | A        | <b>B</b> | C        | D        | E        | F |
| Q5  | <b>A</b> | B        | C        | D        | E        | F |
| Q6  | A        | B        | C        | <b>D</b> | E        | F |
| Q7  | A        | <b>B</b> | C        | D        | E        | F |
| Q8  | A        | B        | <b>C</b> | D        | E        | F |
| Q9  | A        | <b>B</b> | C        | D        | E        | F |
| Q10 | A        | B        | C        | <b>D</b> | E        | F |
| Q11 | A        | <b>B</b> | C        | D        | E        | F |
| Q12 | A        | B        | <b>C</b> | D        | E        | F |
| Q13 | <b>A</b> | B        | C        | D        | E        | F |
| Q14 | A        | B        | C        | <b>D</b> | E        | F |



It shows a two-cell battery, with a variable resistor, and an LED connected in series.

It shows a two-cell battery, with a fixed resistor, and an LED connected in series.

It shows a two-cell battery, with a diode, and an LED connected in series.

It shows a three-cell battery, with a fixed resistor, and an LED connected in series.

It shows a two-cell battery, with a fixed resistor, and an LED connected in parallel.

It shows a two-cell battery, with a fixed resistor, and a light bulb connected in series.

1. According to Circuit Diagram 1, what does E represent in the circuit diagram?  
[1]

A 5 Ohm variable resistor

A 5 Amp ammeter

A 5 Volt battery

A 5 Ohm light bulb

**A 5 Ohm resistor**

A fuse

2. What does this circuit diagram show?  
[1]

3. According to Circuit Diagram 1, what does B represent in the circuit diagram?  
[1]

**Negative terminal**

Positive terminal


Fuse

Battery

Ammeter

Voltmeter

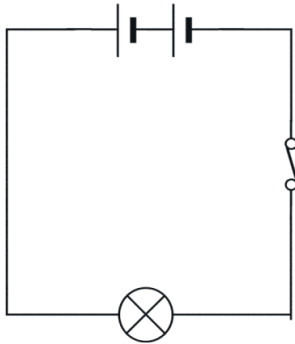4. What does this circuit diagram show?  
[1]



It shows a two-cell battery, with a closed switch and a fixed resistor connected in series.

It shows a two-cell battery, with a closed switch and a light bulb connected in series.


It shows a two-cell battery, with an open switch and a light bulb connected in series.

It shows a two-cell battery, with a fuse and a light bulb connected in series.

It shows a one-cell battery, with a closed switch and a light bulb connected in series.

It shows a two-cell battery, with a closed switch and a light bulb connected in parallel.

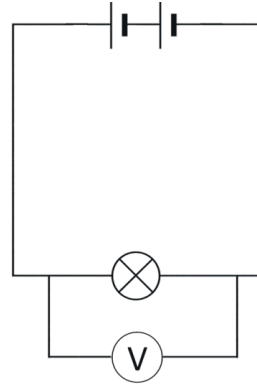5. What does this circuit diagram show?  
[1]



It shows a two-cell battery, with a lamp in series, and a voltmeter in parallel measuring the voltage of the lamp.

It shows a one-cell battery, with a lamp in series, and a voltmeter in parallel.


It shows a two-cell battery, with a lamp in series, and an ammeter in series.

It shows a two-cell battery, with a lamp in series, and a voltmeter in series.

It shows a two-cell battery, with a lamp in series, and an ohmmeter in parallel.

It shows a two-cell battery, with a resistor in series, and a voltmeter in parallel.

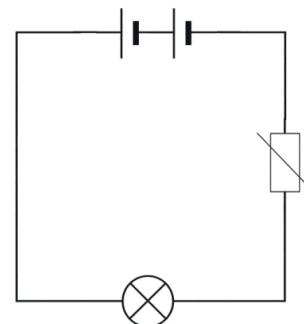6. What does this circuit diagram show?  
[1]



It shows a two-cell battery, with a thermistor and a bulb.


It shows a two-cell battery, with a light-dependent resistor (LDR) and a bulb.

It shows a two-cell battery, with a fixed resistor and a bulb.

It shows a two-cell battery, with a variable resistor and a bulb.

It shows a one-cell battery, with a variable resistor and a bulb.

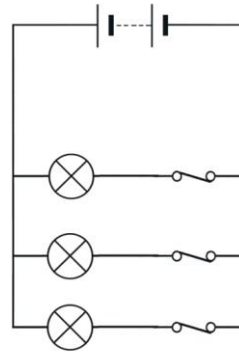It shows a two-cell battery, with a potentiometer and a motor.



It shows a two-cell battery, and three resistors all in parallel with a closed switch for each resistor.

It shows a two-cell battery, and three bulbs all in parallel with one master switch.

It shows a two-cell battery, and three bulbs all in parallel with a closed switch for each bulb.

It shows a two-cell battery, and three bulbs all in series with a closed switch for each bulb.

It shows a two-cell battery, and two bulbs all in parallel with a closed switch for each bulb.

It shows a three-cell battery, and three bulbs all in parallel with a closed switch for each bulb.

7. According to Circuit Diagram 1, what does D represent in the circuit diagram?  
[1]

A resistor

A light bulb

A diode


A capacitor

A switch

A motor

8. What does this circuit diagram show?  
[1]

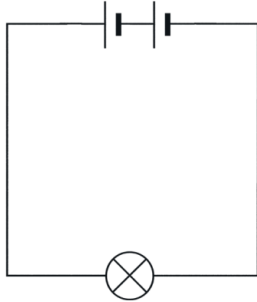9. What does this circuit diagram show?  
[1]



Negative terminal

Positive terminal

An open switch

A light bulb

It shows a two-cell battery with an LED connected in series.

It shows a two-cell battery with a light bulb connected in series.


It shows a three-cell battery with a light bulb connected in series.

It shows a one-cell battery with a light bulb connected in series.

It shows a two-cell battery with a fixed resistor connected in series.

It shows a two-cell battery with a light bulb connected in parallel.

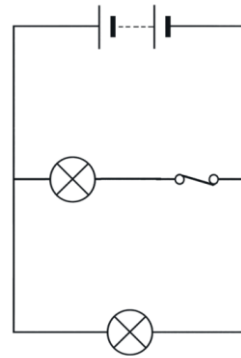11. What does this circuit diagram show?  
[1]



It shows a two-cell battery, with two lamps connected in parallel, and one open switch in the main branch.

It shows a two cell battery, with two lamps connected in parallel, and one closed switch in the first path, which can switch one lamp off.


It shows a two-cell battery, with two lamps connected in parallel, and a switch for each lamp.

It shows a two-cell battery, with one lamp and one motor connected in parallel.

It shows a three-cell battery, with two lamps connected in parallel, and one closed switch.

It shows a two-cell battery, with two lamps connected in series, and one closed switch.

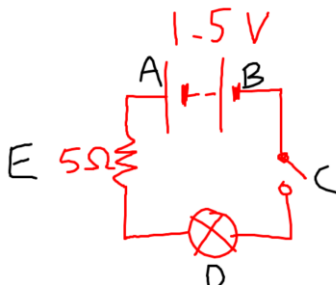10. The following 5 questions refer to Circuit Diagram 1, what does A represent in the circuit diagram? [1]



A 5 Ohm resistor

A closed switch

12. What is wrong with this circuit diagram? [1]



The battery is backwards.

The switch is in the wrong position.


It is not connected, so electricity won't flow.

The bulb is broken.

There is a short circuit.

The voltage is too high for the components.

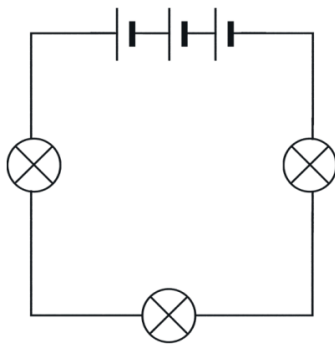13. What does this circuit diagram show? [1]



It shows a three-cell battery, with three light bulbs connected in series.

It shows a three-cell battery, with three light bulbs connected in parallel.

It shows a single-cell battery, with three light bulbs connected in series.

It shows a two-cell battery, with three light bulbs connected in series.

It shows a three-cell battery, with three fixed resistors connected in series.

It shows a three-cell battery, with two light bulbs connected in series.

14. According to Circuit Diagram 1, what does C represent in the circuit diagram? [1]

A closed switch

A motor

A wire

An open switch

A buzzer

A cell