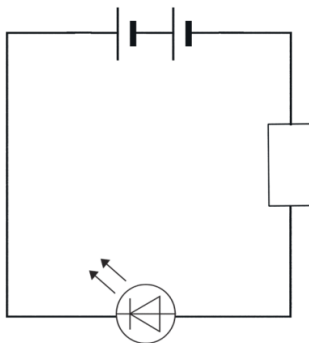


Q1	A	B	C	D	E	F
Q2	A	B	C	D	E	F
Q3	A	B	C	D	E	F
Q4	A	B	C	D	E	F
Q5	A	B	C	D	E	F
Q6	A	B	C	D	E	F
Q7	A	B	C	D	E	F
Q8	A	B	C	D	E	F
Q9	A	B	C	D	E	F
Q10	A	B	C	D	E	F
Q11	A	B	C	D	E	F
Q12	A	B	C	D	E	F
Q13	A	B	C	D	E	F
Q14	A	B	C	D	E	F

1. According to Circuit Diagram 1, what does E represent in the circuit diagram?

- A. A 5 Ohm variable resistor
- B. A 5 Amp ammeter
- C. A 5 Volt battery
- D. A 5 Ohm light bulb
- E. A 5 Ohm resistor
- F. A fuse

2. What does this circuit diagram show?



A. It shows a two-cell battery, with a variable resistor, and an LED connected in series.

B. It shows a two-cell battery, with a fixed resistor, and an LED connected in series.

C. It shows a two-cell battery, with a diode, and an LED connected in series.

D. It shows a three-cell battery, with a fixed resistor, and an LED connected in series.


E. It shows a two-cell battery, with a fixed resistor, and an LED connected in parallel.

F. It shows a two-cell battery, with a fixed resistor, and a light bulb connected in series.

3. According to Circuit Diagram 1, what does B represent in the circuit diagram?

- A. Negative terminal
- B. Positive terminal
- C. Fuse
- D. Battery
- E. Ammeter
- F. Voltmeter

4. What does this circuit diagram show?

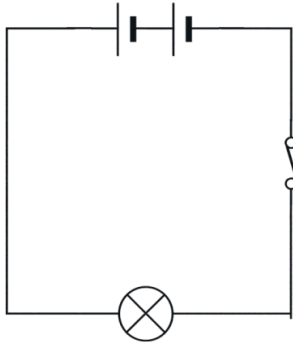

A. It shows a two-cell battery, with a closed switch and a fixed resistor connected in series.

B. It shows a two-cell battery, with a closed switch and a light bulb connected in series.


C. It shows a two-cell battery, with an open switch and a light bulb connected in series.

D. It shows a two-cell battery, with a fuse and a light bulb connected in series.

E. It shows a one-cell battery, with a closed switch and a light bulb connected in series.

F. It shows a two-cell battery, with a closed switch and a light bulb connected in parallel.

5. What does this circuit diagram show?

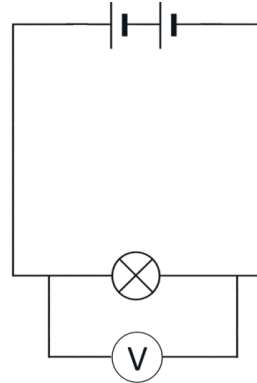

A. It shows a two-cell battery, with a lamp in series, and a voltmeter in parallel measuring the voltage of the lamp.

B. It shows a one-cell battery, with a lamp in series, and a voltmeter in parallel.


C. It shows a two-cell battery, with a lamp in series, and an ammeter in series.

D. It shows a two-cell battery, with a lamp in series, and a voltmeter in series.

E. It shows a two-cell battery, with a lamp in series, and an ohmmeter in parallel.

F. It shows a two-cell battery, with a resistor in series, and a voltmeter in parallel.

6. What does this circuit diagram show?

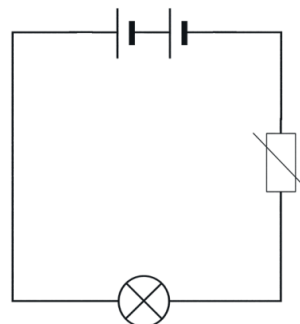

A. It shows a two-cell battery, with a thermistor and a bulb.

B. It shows a two-cell battery, with a light-dependent resistor (LDR) and a bulb.

C. It shows a two-cell battery, with a fixed resistor and a bulb.

D. It shows a two-cell battery, with a variable resistor and a bulb.


E. It shows a one-cell battery, with a variable resistor and a bulb.

F. It shows a two-cell battery, with a potentiometer and a motor.

7. According to Circuit Diagram 1, what does D represent in the circuit diagram?

- A. A resistor
- B. A light bulb
- C. A diode
- D. A capacitor
- E. A switch
- F. A motor

8. What does this circuit diagram show?

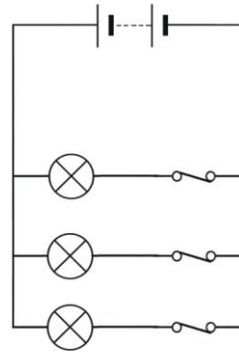

A. It shows a two-cell battery, and three resistors all in parallel with a closed switch for each resistor.

B. It shows a two-cell battery, and three bulbs all in parallel with one master switch.


C. It shows a two-cell battery, and three bulbs all in parallel with a closed switch for each bulb.

D. It shows a two-cell battery, and three bulbs all in series with a closed switch for each bulb.

E. It shows a two-cell battery, and two bulbs all in parallel with a closed switch for each bulb.


F. It shows a three-cell battery, and three bulbs all in parallel with a closed switch for each bulb.

9. What does this circuit diagram show?

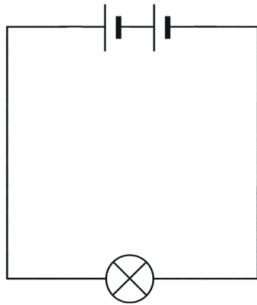

- A. It shows a two-cell battery with an LED connected in series.
- B. It shows a two-cell battery with a light bulb connected in series.
- C. It shows a three-cell battery with a light bulb connected in series.
- D. It shows a one-cell battery with a light bulb connected in series.
- E. It shows a two-cell battery with a fixed resistor connected in series.
- F. It shows a two-cell battery with a light bulb connected in parallel.

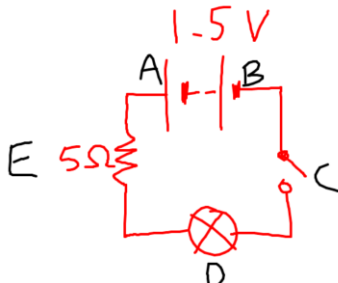
10. The following 5 questions refer to Circuit Diagram 1, what does A represent in the circuit diagram?



- A. A 5 Ohm resistor
- B. A closed switch

- C. Negative terminal
- D. Positive terminal
- E. An open switch
- F. A light bulb

11. What does this circuit diagram show?

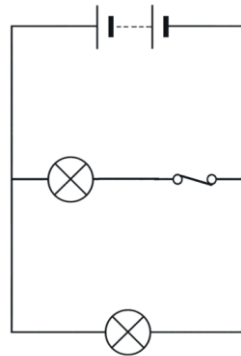


- A. It shows a two-cell battery, with two lamps connected in parallel, and one open switch in the main branch.
- B. It shows a two cell battery, with two lamps connected in parallel, and one closed switch in the first path, which can switch one lamp off.
- C. It shows a two-cell battery, with two lamps connected in parallel, and a switch for each lamp.
- D. It shows a two-cell battery, with one lamp and one motor connected in parallel.
- E. It shows a three-cell battery, with two lamps connected in parallel, and one closed switch.
- F. It shows a two-cell battery, with two lamps connected in series, and one closed switch.

12. What is wrong with this circuit diagram?



- A. The battery is backwards.
- B. The switch is in the wrong position.
- C. It is not connected, so electricity won't flow.
- D. The bulb is broken.
- E. There is a short circuit.
- F. The voltage is too high for the components.

13. What does this circuit diagram show?

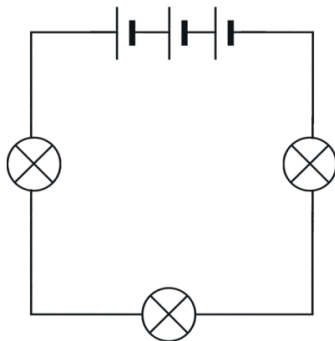

- A. It shows a three-cell battery, with three light bulbs connected in series.
- B. It shows a three-cell battery, with three light bulbs connected in parallel.

C. It shows a single-cell battery, with three light bulbs connected in series.

D. It shows a two-cell battery, with three light bulbs connected in series.

E. It shows a three-cell battery, with three fixed resistors connected in series.

F. It shows a three-cell battery, with two light bulbs connected in series.

14. According to Circuit Diagram 1, what does C represent in the circuit diagram?

- A. A closed switch
- B. A motor
- C. A wire
- D. An open switch
- E. A buzzer
- F. A cell