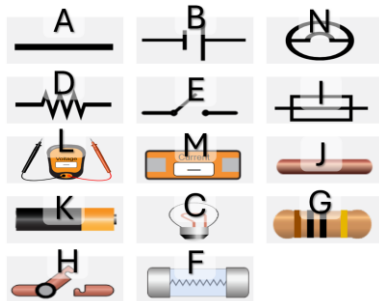


Match the following terms to the correct example:



Word Bank: Ammeter, Voltmeter, Fuse, Light Bulb, Cell, Switch, Wire, Resistor

1. A _____

2. B _____

3. C _____

4. D _____

5. E _____

6. F _____

7. G _____

8. H _____

9. I _____

10. J _____

11. K _____

12. L _____

13. M _____

14. N _____