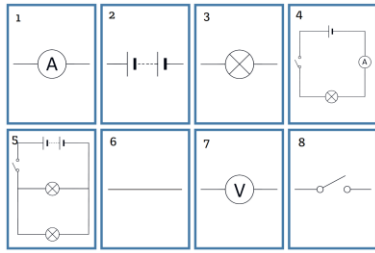


Match the following to the correct example:



Word Bank: series circuit, GDP, voltmeter, bulb, ammeter, parallel circuit, Iodine, battery, wire, LPG, switch, GPT

1. 1 _____

2. 2 _____

3. 3 _____

4. 4 _____

5. 5 _____

6. 6 _____

7. 7 _____

8. 8 _____

10. 10 _____

11. 11 _____

12. 12 _____


13. 13 _____

14. 14 _____

15. 15 _____

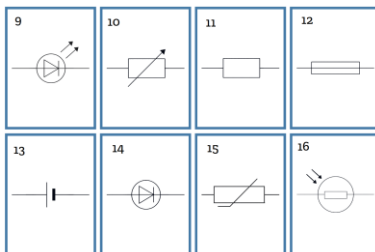16. 16 _____

Match the following to the correct example:



Word Bank: variable resistor, GPT, fixed resistor, thermistor, LPG, fuse, Iodine, diode, cell, GDP, LED, LDR

9. 9 _____